

Problem 1: Denard Scaling

Power density stays constant, $\frac{P}{A} = \frac{dCv^2f}{\text{area}}$

$$A' = A/s^2$$

all of this assumes $S > 1 \Rightarrow S = \frac{1}{k}$ where $k=0.7$

$$\text{so } (\text{Power})' = dCv^2f (s^2) \longrightarrow \text{new power} = (P)(0.7)^2$$

$$C' = C/s \text{ ; can ignore } d \text{ ; } V' = V/s$$

$$\boxed{P' = 9.8W} \quad (2.5 \text{ pts})$$

so! $P' = d \cdot s \cdot C' \cdot \frac{1}{s^2} \cdot V'^2 \cdot f \cdot s^2$

$$P' = d \cdot C' \cdot V'^2 \cdot (f \cdot s) \quad \text{so } f \text{ will scale with } s \rightarrow$$

$$\boxed{f' = f(0.7) = 5.7 \text{ GHz}} \quad (2.5 \text{ pts})$$

Problem 2: Noise Margins

answers may vary due to nature of plot,
it's just important for the numbers to be
generally correct

$$V_{OH} = \sim 1.7V$$

$$V_{OL} = \sim 0.3V$$

$$V_{IH} = \sim 1.3V$$

$$V_{IL} = \sim 0.7V$$

3 pt

$$\text{Noise Margin (H)} = NM_H = V_{OH} - V_{IH} = \sim 0.4V$$

$$\text{Noise Margin (L)} = NM_L = V_{IL} - V_{OL} = \sim 0.4V$$



2 pt

Problem 3



(1) black box implements NAND gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

(1 pt)

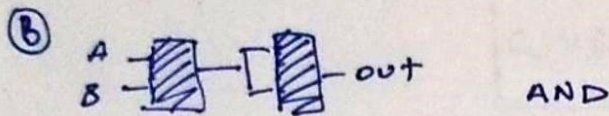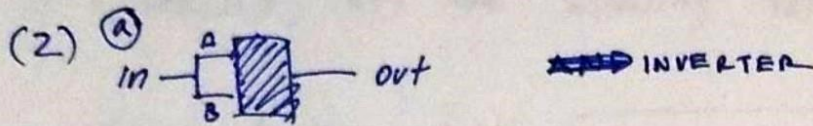

(2 pt)

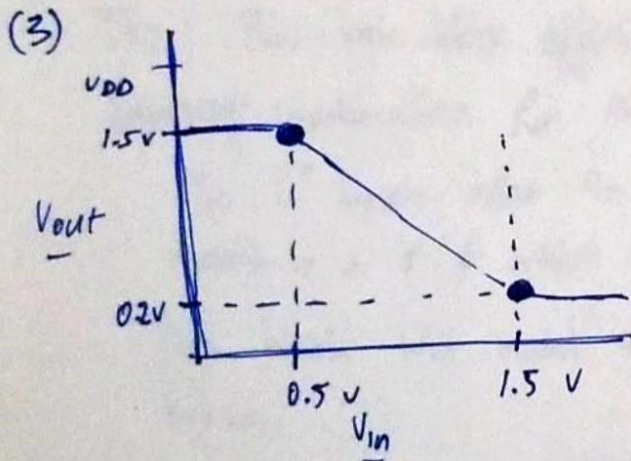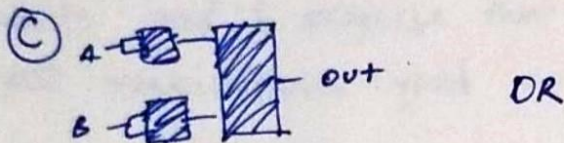

sorry for the messiness;
it's okay if the don't
show V_{DD} . Most important
for the students to draw
the slope = -1 points (dark dots)

(1 pt)

(4) propagation delay is $5\mu s$

(given number accounts for rise time & 50%
& what not)

Problem 4

(1) • $XNOR(A, B)$ has the following truth table

A	B	Y	
0	0	1	C_0
0	1	0	C_1
1	0	0	C_2
1	1	1	C_3

(2.5 pt)

• Based of truth table ! $C_0 = 1, C_2 = 1$
 $C_1 = 0, C_3 = 0$

Students need to recognize that " C_i " inputs allow them to select which input combinations yield a 0 & which ones yield a 1.

(2) Yes! This logic block effectively models every possible input ~~sum~~ of combination for the inputs (A & B).

The " C " inputs allow the user to pick which input combination results in a 1 & which combinations ~~that~~ result in 0.

This block will model any combinational function in sum-of-product form.

Any explanation that touches on any of these should get credit

2.5 pts

Problem 5

- (1) STUDENTS may write out entire truth table ... that's too much work for me but great for them. They could also simplify expression first.

$$\begin{aligned}
 & \overline{(AB)(C\bar{D} + \bar{C}D)(E+F)} = \\
 & \overline{AB} + \overline{(C\bar{D} + \bar{C}D)} + \overline{(E+F)} = \\
 & A + \bar{B} + (\bar{C} + D)(C + \bar{D}) + \bar{E} + \bar{F} = \\
 & \underline{A + \bar{B} + \bar{C}\bar{D} + CD + \bar{E} + \bar{F}}
 \end{aligned}$$

Simpler truth table based off the above expression is

A	B	C	D	E	F	Y
1	X	X	X	X	X	1
X	0	X	X	X	X	1
X	X	0	0	X	X	1
X	X	1	1	X	X	1
X	X	X	X	1	X	1
X	X	X	X	X	1	1
0	0	1	0	0	0	0
0	1	0	0	0	0	0

(2.5 pts)

(2.5 pts)

- (2) Could just present the simplified expression from part 1 or can go the following route:

$$\begin{aligned}
 \bar{Y} &= \bar{A}B\bar{C}\bar{D}\bar{E}\bar{F} + \bar{A}B\bar{C}\bar{D}E\bar{F} \\
 Y &= (\bar{A}B\bar{C}\bar{D}\bar{E}\bar{F} + \bar{A}B\bar{C}\bar{D}E\bar{F}) \rightarrow Y = (A + \bar{B} + C + \bar{D} + E + F)(A + \bar{B} + \bar{C} + D + \bar{E} + \bar{F}) \\
 &\quad \text{— then simplify to —} \\
 &\quad \underline{Y = A + \bar{B} + \bar{C}\bar{D} + CD + E + F}
 \end{aligned}$$

Problem 6

$$1) ((\bar{A}\bar{B} + C)(A+B)(\overline{B+AC})) = \bar{A}BC$$

$$(\cancel{\bar{A}\bar{B}A} + \cancel{\bar{A}\bar{B}B} + AC + BC)(\overline{B+AC}) = \quad (1.67)$$

$$(AC + BC)(B\bar{A} + B\bar{C}) =$$

$$A\cancel{C}\bar{A}B + \bar{A}B\cancel{B}C + B\bar{C}\cancel{A}C + B\bar{C}\cancel{B}C =$$

$$\bar{A}BC$$

$$= \bar{A}BC \quad \checkmark$$

$$2) \bar{A}\bar{B} + AB + \bar{A}B = \bar{A} + B$$

$$\bar{A}\bar{B} + \bar{A}B + AB =$$

$$\bar{A}(\bar{B} + B) + AB = \bar{A} + B$$

$$\bar{A} + AB + \bar{A}B =$$

$$\bar{A} + B(A + \bar{A}) =$$

$$\bar{A} + B = \bar{A} + B \quad \checkmark$$

(Because you can... why not!)

$$3) \bar{A}(A+B) + (B+\bar{A}\bar{A})(A+\bar{B}) = A+B$$

$$\bar{A}A + \bar{A}B + (B+\bar{A})(A+\bar{B}) =$$

$$\bar{A}B + AB + B\bar{B} + A + A\bar{B} =$$

$$(\bar{A} + A)B + A(1 + \bar{B}) =$$

$$A + B = A + B \quad \checkmark$$

(1.67)